

Advance Power Electronics (315340)

MSBTE Diploma · K-Scheme · Semester 5 (EJ / ET / EX / IE) · Important Questions

How this list was made: Based on MSBTE papers **W-2025** and **S-2026** available on msbte.ac.in (these are the only two K-scheme papers of this course so far, so the sample is small). Every question of both papers was grouped by topic. **High** = asked in both papers, **Medium** = asked in one paper, **Low** = in the K-scheme syllabus but not asked yet. Practice guidance only — not a prediction of the exam.

Most repeated topics

#	Topic	Unit	Times asked
1	Quadrant classification of choppers; Type A / B / C / D operation	2	5 (S-26, W-25)
2	SIT – advantages over BJT/SCR, comparison with MCT	1	3 (S-26, W-25)
3	Snubber circuit / dv/dt and di/dt protection of SCR	1	3 (S-26, W-25)
4	Step-up / step-down chopper using MOSFET (role of MOSFET, comparison)	2	3 (S-26, W-25)
5	Single-phase current source inverter (circuit, working, R load)	3	3 (S-26, W-25)
6	Three-phase VSI – 180° and 120° conduction modes (working, comparison)	3	3 (S-26, W-25)
7	Voltage stabilizer – definition, necessity, block diagram, types	4	3 (S-26, W-25)
8	MCT – symbol, V-I characteristics (also FCT symbol)	1	2 (S-26, W-25)
9	Thermal protection of SCR – need, thermal resistance, heat sink	1	2 (S-26, W-25)
10	PWM – types, advantages, how they differ	3	2 (S-26, W-25)

Unit I – Modern Power Devices and Protection Circuits (10 M)

Question / topic	Marks	Asked in	Probability
SIT – advantages over BJT/SCR, comparison with MCT <ul style="list-style-type: none"> State any two advantages of SIT over BJT. (W-25 Q.1a) State the advantage of SIT over SCR. (S-26 Q.1b) Compare SIT & MCT: switching speed, advantages, disadvantage, application. (S-26 Q.4a) 	2 M, 4 M	S-26, W-25	High
Snubber circuit / dv/dt and di/dt protection of SCR <ul style="list-style-type: none"> List any two components used in a snubber circuit. (W-25 Q.1b) Explain dv/dt protection using R-C snubber circuit. (W-25 Q.3a) Compare di/dt and dv/dt protection circuits used for thyristors. (S-26 Q.3d) 	2 M, 4 M	S-26, W-25	High
MCT – symbol, V-I characteristics (also FCT symbol) <ul style="list-style-type: none"> Draw and explain the V-I characteristics of MCT. (W-25 Q.2a) Draw the symbol of MCT and FCT. (S-26 Q.1f) 	2 M, 4 M	S-26, W-25	High

Thermal protection of SCR – need, thermal resistance, heat sink • State the need of thermal protection in SCRs and define thermal resistance. (W-25 Q.4a) • Explain the role of heat sink in thermal protection of SCR. (S-26 Q.2b)	4 M	S-26, W-25	High
SIT / MCT / FCT construction and working In syllabus, not asked yet — prepare for a surprise question.	—	Not yet	Low

Unit II – DC to DC Converters (16 M)

Question / topic	Marks	Asked in	Probability
Quadrant classification of choppers; Type A / B / C / D operation • Identify a suitable chopper for output in first and second quadrant and explain its operation. (W-25 Q.3b) • Explain the operation of a Type-C (two-quadrant Type-A) chopper with diagram. (W-25 Q.4b) • Classify the chopper on quadrant operation and explain second quadrant chopper. (W-25 Q.5a) • Explain Type A chopper with circuit & waveform. (S-26 Q.2a) • Draw a neat circuit of Type D chopper and explain its operation with waveform. (S-26 Q.3c)	4 M, 6 M	S-26, W-25	High
Step-up / step-down chopper using MOSFET (role of MOSFET, comparison) • State the role of MOSFET in chopper circuit. (W-25 Q.1d) • Compare step-up & step-down chopper: output voltage, duty cycle. (S-26 Q.1g) • Explain step-up chopper using MOSFET with waveform. (S-26 Q.4b)	2 M, 4 M	S-26, W-25	High
Chopper – functions, principle, block diagram • State the functions of chopper (any two points). (W-25 Q.1c) • Explain the function of a DC chopper with a neat block diagram. (W-25 Q.2b)	2 M, 4 M	W-25	Medium
Chopper control strategies (TRC, CLC) • State the control strategies used in chopper. (S-26 Q.1d)	2 M	S-26	Medium
SMPS – types, block diagram, advantages over linear supply • State the types of SMPS & explain block diagram of SMPS with its advantages over linear power supply. (S-26 Q.6a)	6 M	S-26	Medium
Type E (four-quadrant) chopper; flyback and push-pull converters In syllabus, not asked yet — prepare for a surprise question.	—	Not yet	Low

Unit III – Multi Level Inverters (16 M)

Question / topic	Marks	Asked in	Probability
Single-phase current source inverter (circuit, working, R load) <ul style="list-style-type: none"> • Draw neat labelled circuit of a single phase CSI. (W-25 Q.1e) • Describe the working principle of current source inverter. (W-25 Q.2c) • Explain the working of single phase CSI with resistive load. (S-26 Q.3a) 	2 M, 4 M	S-26, W-25	High
Three-phase VSI – 180° and 120° conduction modes (working, comparison) <ul style="list-style-type: none"> • Compare 120° conduction mode with 180° conduction mode of 3-phase VSI (any four points). (W-25 Q.5b) • Explain the difference in switching patterns between 180° & 120° conduction mode. (S-26 Q.4c) • Explain working of three phase VSI with resistive load for 180° conduction mode with circuit diagram. (S-26 Q.5a) 	4 M, 6 M	S-26, W-25	High
PWM – types, advantages, how they differ <ul style="list-style-type: none"> • Name two types of PWM techniques and state any two advantages of PWM in inverters. (W-25 Q.4c) • What is pulse modulation? List various PWM techniques & state how they differ. (S-26 Q.5b) 	4 M, 6 M	S-26, W-25	High
Inverter – definition, classification, applications <ul style="list-style-type: none"> • Define inverter & give the classification of the inverter. (S-26 Q.1a) • State the application of inverter. (S-26 Q.1e) 	2 M	S-26	Medium
Comparison of VSI and CSI <ul style="list-style-type: none"> • Compare VSI & CSI: input source, output controlled, commutation circuit, protection. (S-26 Q.2d) 	4 M	S-26	Medium
Sinusoidal PWM (SPWM) with waveforms <ul style="list-style-type: none"> • Explain the working of sinusoidal PWM (SPWM) with suitable waveforms. (W-25 Q.6a) 	6 M	W-25	Medium
Multiple-pulse PWM (MPWM) In syllabus, not asked yet — prepare for a surprise question.	—	Not yet	Low

Unit IV – AC Voltage Stabilizer and UPS (12 M)

Question / topic	Marks	Asked in	Probability
Voltage stabilizer – definition, necessity, block diagram, types <ul style="list-style-type: none"> • Define voltage stabilizer and state the necessity of stabilizer. (W-25 Q.2d) • Draw the basic block diagram of AC voltage stabilizer. (S-26 Q.1c) 	2 M, 4 M	S-26, W-25	High

<ul style="list-style-type: none"> List different types of stabilizers and explain servo type stabilizer. (S-26 Q.2c) 			
Servo type voltage stabilizer <ul style="list-style-type: none"> Explain the working principle of a servo stabilizer with neat diagram. (W-25 Q.3c) ... explain servo type of stabilizer with suitable diagram. (S-26 Q.2c) 	4 M	S-26, W-25	High
UPS specifications / on-line vs off-line UPS <ul style="list-style-type: none"> Describe the specification of UPS: response time, output frequency, load power factor. (W-25 Q.6b) Compare online & offline UPS on six specifications. (S-26 Q.6c) 	6 M	S-26, W-25	High
Relay type voltage stabilizer <ul style="list-style-type: none"> Explain the relay type stabilizer with neat diagram. (S-26 Q.4d) 	4 M	S-26	Medium
Rechargeable batteries – Li-ion, NMC, NCA classification <ul style="list-style-type: none"> Explain the classification of Li-Ion, NMC and NCA batteries. (W-25 Q.4d) 	4 M	W-25	Medium
Static voltage stabilizer; battery backup time and transfer time In syllabus, not asked yet — prepare for a surprise question.	—	Not yet	Low

Unit V – Electric Drives and Industrial Applications (16 M)

Question / topic	Marks	Asked in	Probability
Variable frequency drive (VFD) – definition, necessity, block diagram <ul style="list-style-type: none"> Define VFD and state necessity of VFD. (W-25 Q.1f) What is VFD? Explain the block diagram of VFD. (S-26 Q.3b) 	2 M, 4 M	S-26, W-25	High
Charge controller in PV system – function, block diagram <ul style="list-style-type: none"> Draw the block diagram of a charge controller and explain. (W-25 Q.3d) State the function of charge controller in PV systems; explain its block diagram. (S-26 Q.4e) 	4 M	S-26, W-25	High
AC-to-AC converter with DC link in wind power generation <ul style="list-style-type: none"> Explain the block diagram of AC to AC converter using DC link in wind power generation. (W-25 Q.4e) Explain the use of AC-to-AC converter in wind power generation with suitable diagram. (S-26 Q.5c) 	4 M, 6 M	S-26, W-25	High
Electric vehicles – PHEV / PEV block diagram, comparison <ul style="list-style-type: none"> With neat block diagram explain construction and working of PHEV. (W-25 Q.6c) Explain the block diagram of PEV; compare PEV & PHEV. (S-26 Q.6b) 	6 M	S-26, W-25	High

Electrical traction system – working, applications • State any two applications of electrical traction system. (W-25 Q.1g) • Explain the working of an electrical traction system with neat labelled diagram. (W-25 Q.5c)	2 M, 6 M	W-25	Medium
EV control unit and drive mechanism In syllabus, not asked yet — prepare for a surprise question.	—	Not yet	Low

Exam tips from the two papers

- **Choppers carry the most marks:** quadrant classification and Type A / B / C / D circuits came 5 times in two papers. Practise each circuit with its output voltage and current waveforms and the quadrant it works in.
- Both papers asked the **single-phase CSI, three-phase VSI (180° / 120°)** and **PWM types**. Learn the gating sequence S1-S6 and draw the six-step waveform neatly.
- Unit V is all block diagrams: **VFD, PV charge controller, wind AC-DC-AC converter, PEV / PHEV** — each was asked in both papers. Draw clean labelled blocks with arrows.
- **Servo stabilizer** and **UPS specifications (on-line vs off-line)** appeared in both papers; prepare the comparison table on at least six points.
- Neither paper had numericals. Simple calculations (duty cycle, $V_o = D \cdot V_s$, $V_o = V_s / (1-D)$, junction temperature, SPWM modulation index) are included in our model papers only for practice of concepts.
- One S-26 question (Q.2c) covers both 'types of stabilizer' and 'servo stabilizer', so it is counted in both topics.

Note: This is a **important-question list prepared by Ananda Technologies** only for practice and exam preparation, based on the pattern of previous MSBTE question papers and the K-scheme syllabus. It is **not an official MSBTE paper**, and it does **not** mean that these questions will come in the exam. Answers follow standard textbook points; marks shown are indicative. Free for students — anandatechnologies.in