

Power System Operation and Control (315336)

MSBTE Diploma · K-Scheme · Model Question Paper — Set C

Time: 3 Hours**Max. Marks: 70****Instructions:**

1. All questions are compulsory.
2. Answer each next main question on a new page.
3. Illustrate your answers with neat sketches wherever necessary.
4. Figures to the right indicate full marks.
5. Assume suitable data, if necessary.
6. Use of Non-programmable Electronic Pocket Calculator is permissible.
7. Mobile phone, pager and any other electronic communication devices are not permissible in the examination hall.

Q.1 Attempt any FIVE of the following:**10**

- a) State any four main components of a power system.
- b) Write the formula for converting a per unit impedance from an old base to a new base. Explain the terms.
- c) State any two adverse effects of frequency variation on generating plants.
- d) List any four effects of reactive power imbalance in a power system.
- e) Define power system stability and instability.
- f) Give two examples each of small disturbance and large disturbance in a power system.
- g) Name the types of load dispatch centres in India.

Q.2 Attempt any THREE of the following:**12**

- a) Explain the requirements of stable operation of a power system.
- b) Explain the need of constant supply voltage for consumers.
- c) Describe the functioning of automatic voltage regulator (AVR) with a neat block diagram.
- d) State the adverse effects of power system instability.

Q.3 Attempt any THREE of the following:**12**

- a) Derive the relation between real power balance and frequency of a power system.
- b) Explain the unified power flow controller (UPFC) and interline power flow controller (IPFC) with diagrams.
- c) Explain any four methods of improving the transient stability of a power system.
- d) Describe the need of load forecasting in power system operation.

Q.4 Attempt any THREE of the following:

12

- State the concept of reactive power compensation. Name any four reactive power compensating equipments.
- Draw and explain the block diagram of automatic load frequency control (ALFC) with integral control.
- Define dynamic stability. State the methods to improve the dynamic stability limit.
- Explain environmental and social factors in load forecasting.
- State the need and importance of a load dispatch centre.

Q.5 Attempt any TWO of the following:

12

- Draw the per unit reactance diagram for the power system shown below. Choose a base of 50 MVA and 220 kV in the transmission line circuit.

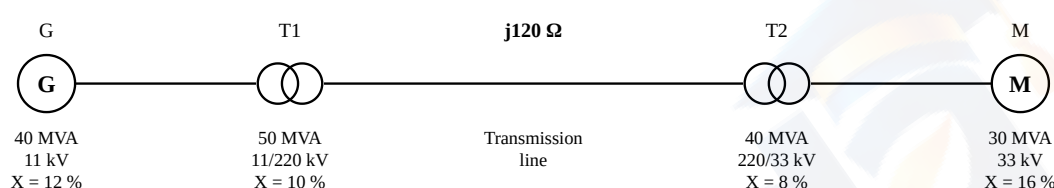


Fig. for Q.5 (a)

- Explain shunt compensation and series compensation methods of reactive power compensation for a transmission line.
- Draw the block diagram of automatic generation control (AGC) for a generating system. Name its components and explain its working.

Q.6 Attempt any TWO of the following:

12

- Derive the relation between voltage and reactive power flow in a simple two-bus system. A load of 0.6 pu active and 0.3 pu reactive power at 1.0 pu voltage is supplied through a line of reactance 0.3 pu. Find the sending-end voltage and the load angle.
- Describe the working of the turbine speed governing system for turbo-generator speed control with a labelled schematic diagram.
- With reference to the Indian power system, state the types of load dispatch centres. Explain the functions of NLDC, RLDC and SLDC.

Note: This is a **model question paper prepared by Ananda Technologies** only for practice and exam preparation, based on the pattern of previous MSBTE question papers and the K-scheme syllabus. It is **not an official MSBTE paper**, and it does **not** mean that these questions will come in the exam. Answers follow standard textbook points; marks shown are indicative. Free for students — anandatechnologies.in